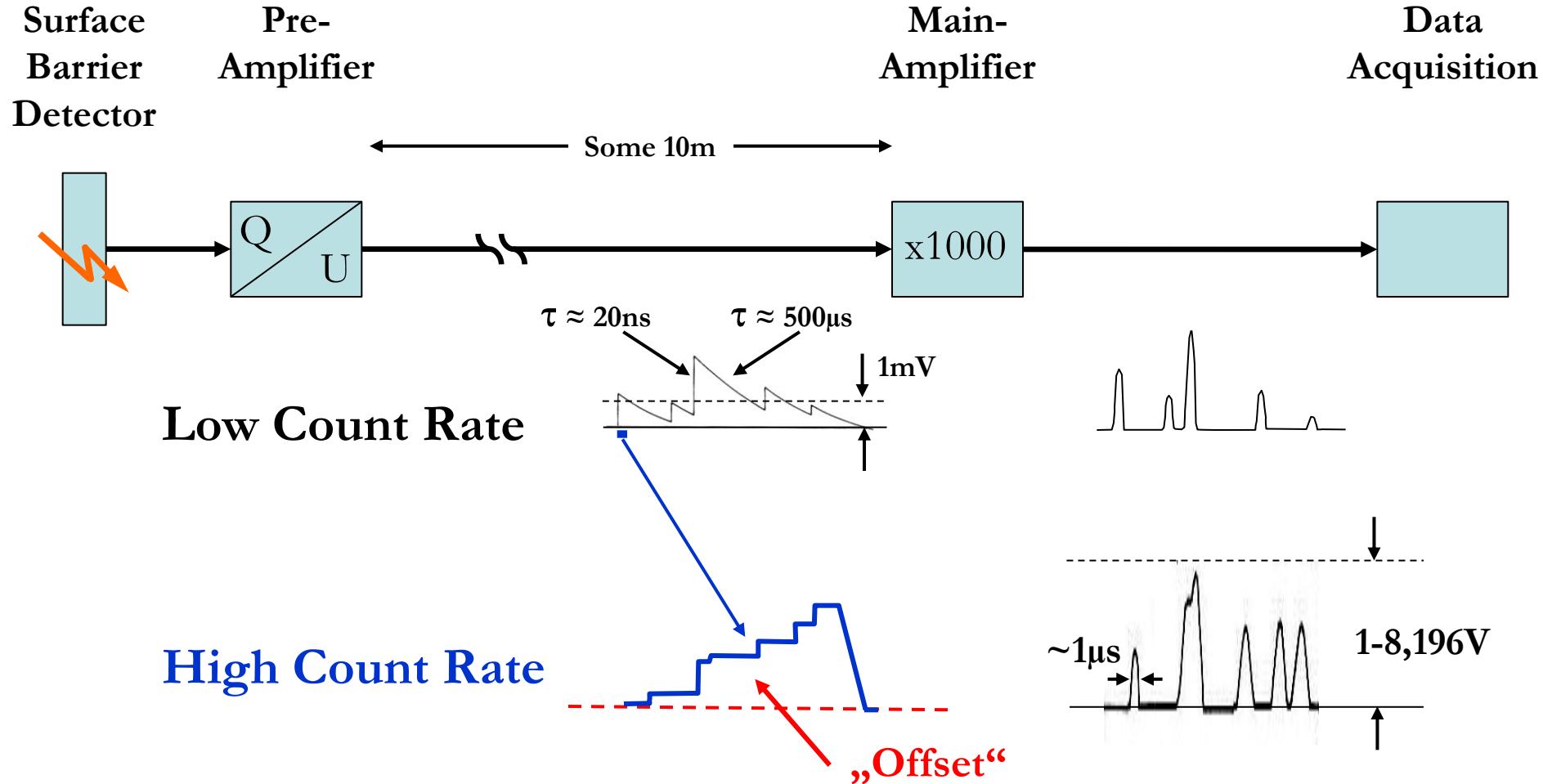


Electronics Outline

- Some Problems from my Diploma Thesis
- Understanding Transfer Functions
- Why does P/Z-Cancellation Work ?
- Why gives a „Bell-Shaped“ Signal the best S/N-Ratio ?
- Summary
- Questions
- Appendices


Electronics

The Amplifier Chain



Electronics

The Main Amplifier

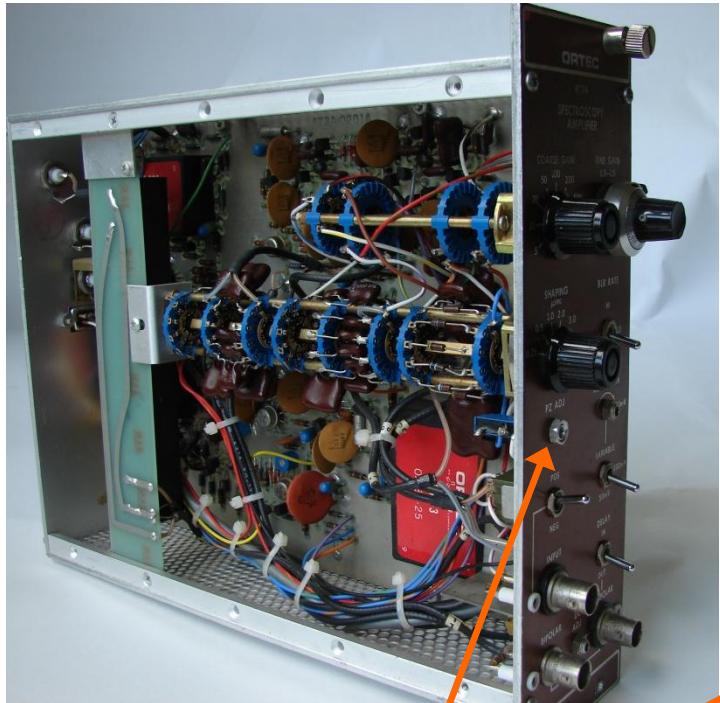


Potentiometer reads P/Z



What does it ?
What does it mean ?
How does the circuit look like ?
How does it work ?




Electronics

The Main Amplifier Input Stage

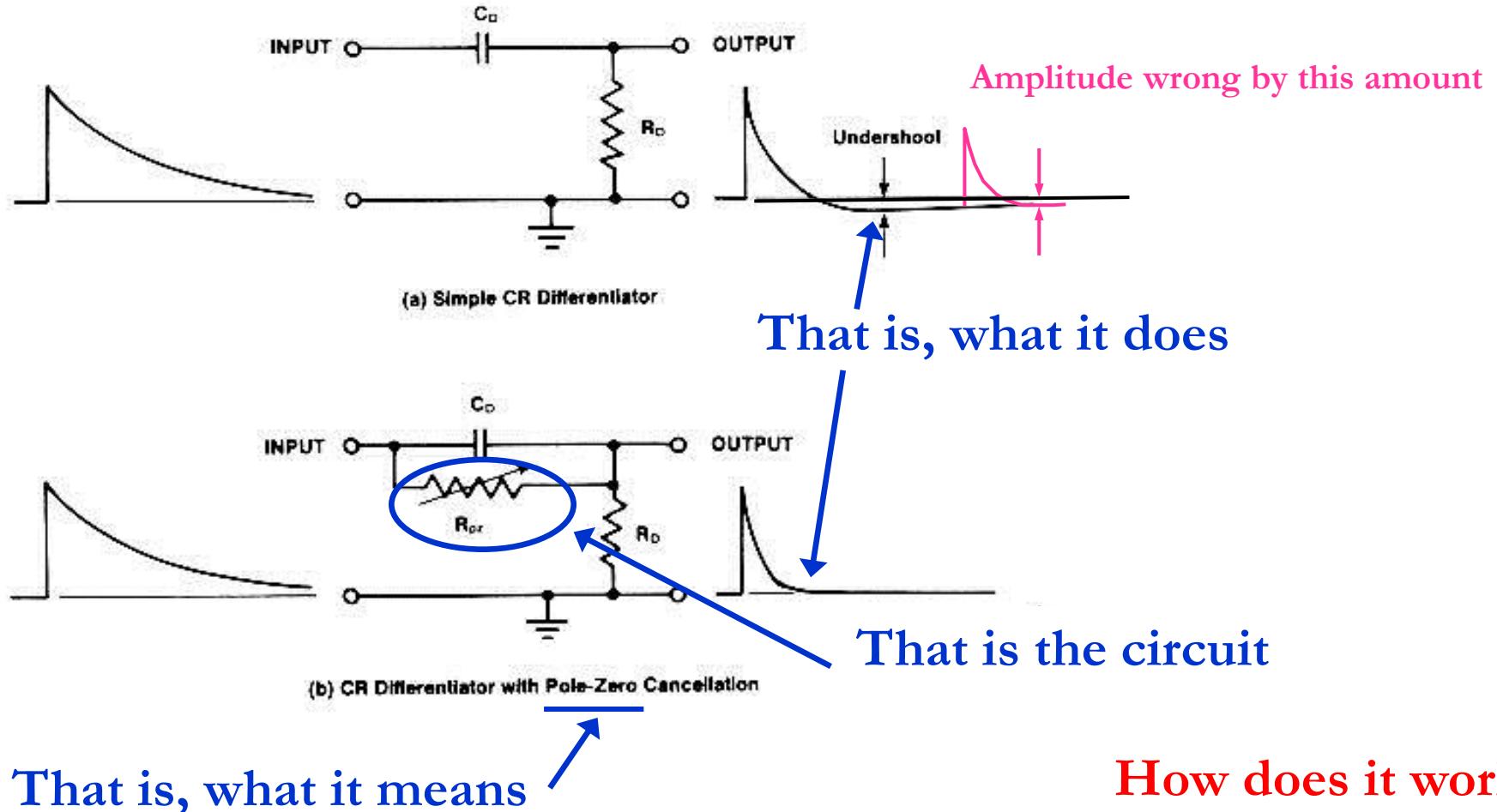

Electronics

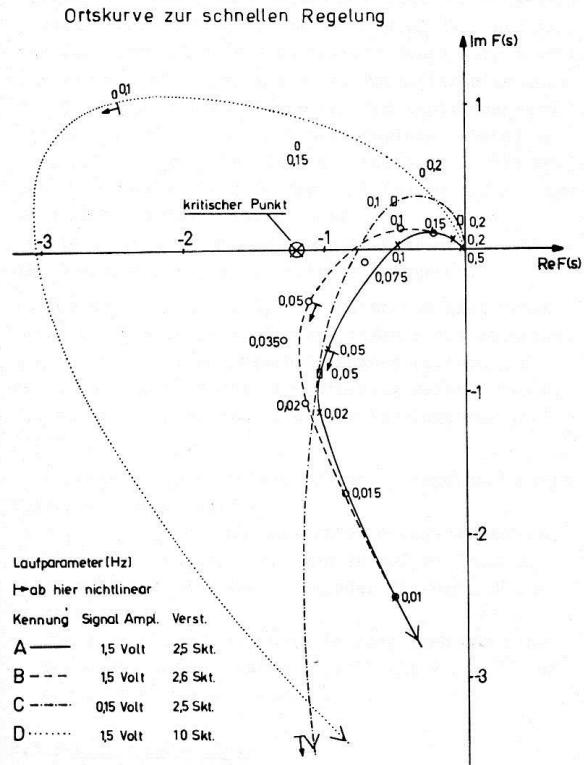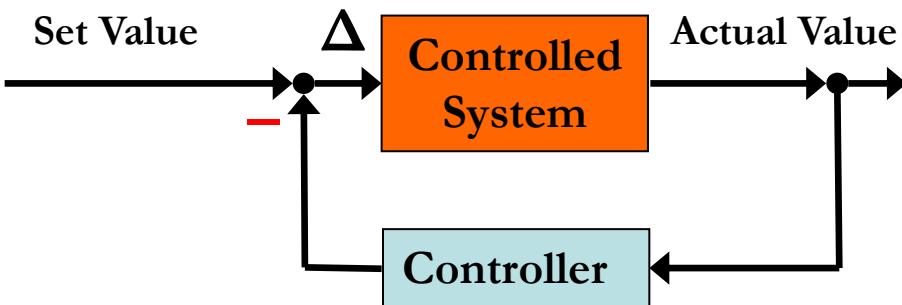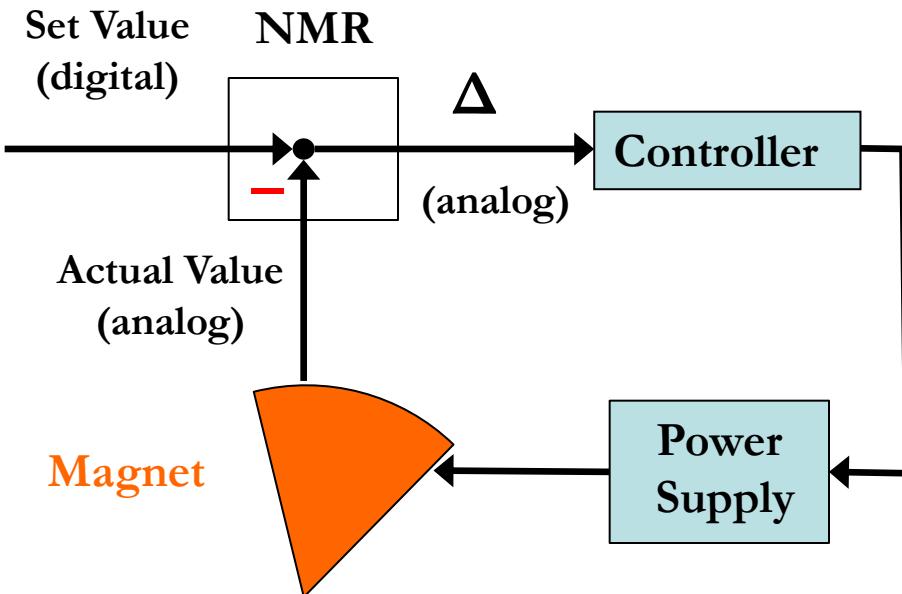NMR Control of a Bending Magnet to $3 \cdot 10^{-6}$





Difficult to interpret


Is there a more compact way to display the dynamics of a system ?

Electronics


Understanding Transfer Functions

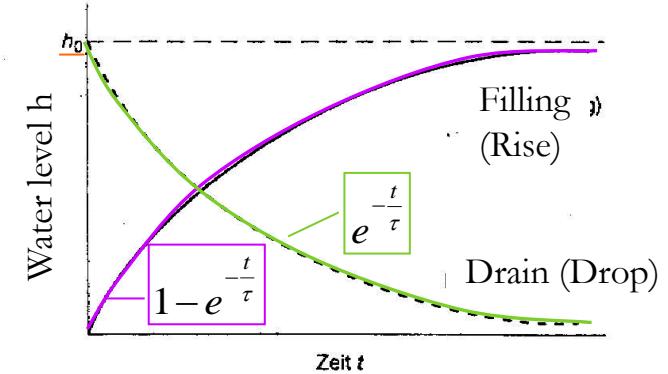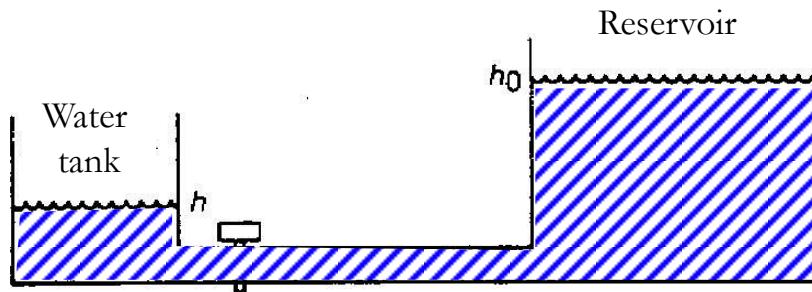

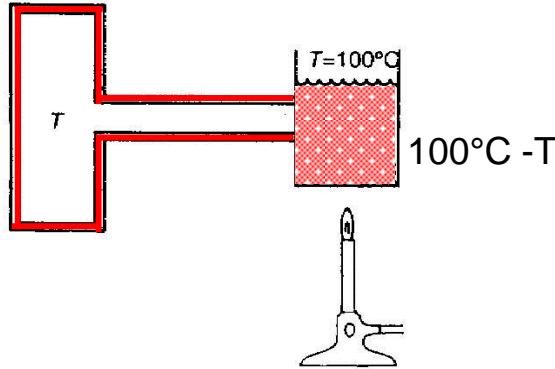- The water tank is filled from a reservoir of unlimited capacity;
- The water level approaches **exponentially** h_0 .



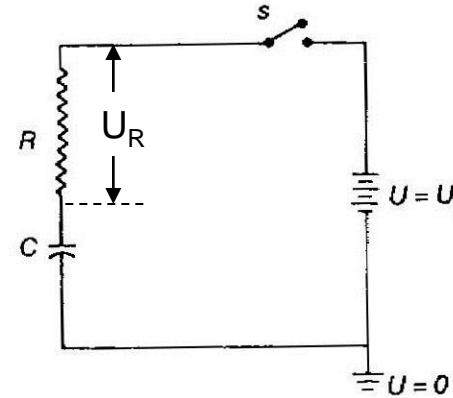The temperature of a piece of metal approaches exponentially 100°C .




The voltage at the capacitor approaches exponentially U_0

Electronics

Understanding Transfer Functions

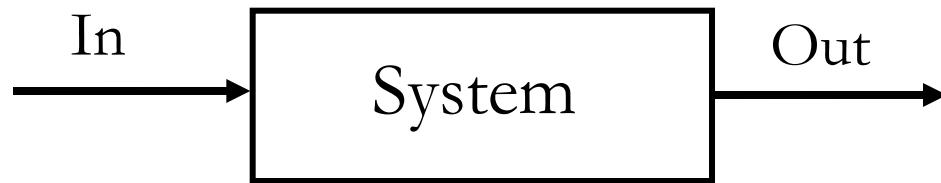How can the dynamics of a linear system be described most efficiently ?




- Refinery
- Aeroplane
- Musical instrument
- Electrical Circuit
- Nucleus

Electronics

Understanding Transfer Functions

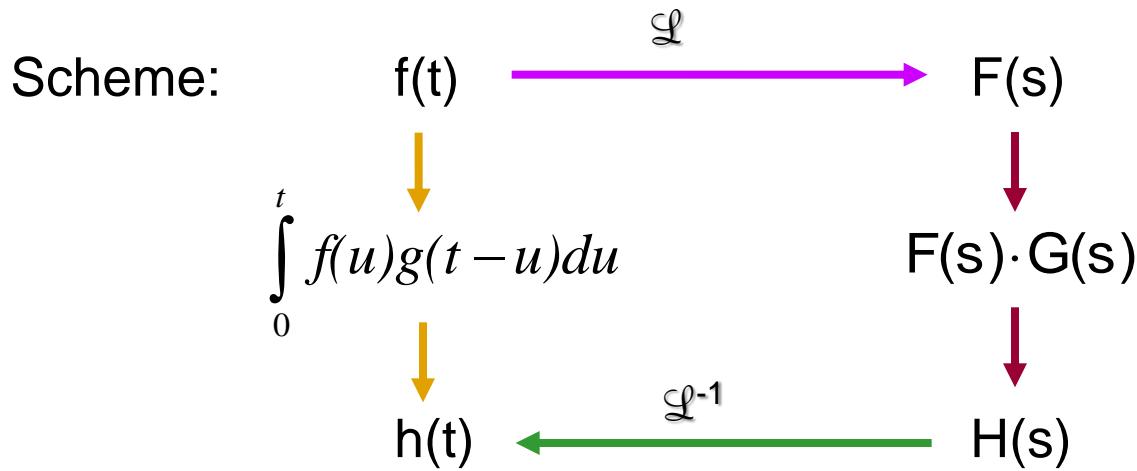- Is a „generalized“ Fourier Transform $f(t) \rightarrow F(s)$ with $s=p+i\omega$
- Is an integral transform, and therefore linear
- „Algebraizes“ linear differential equations
- A convolution in the time domain corresponds to a multiplication of the corresponding Laplace transforms



Electronics

Understanding Transfer Functions

F(s)	f(t)	Remark
$a F_1(s) + b F_2(s)$	$a f_1(t) + b f_2(t)$	Linearity
$s F(s) - f(0)$	$f'(t)$	Derivative
$s^n F(s) - s^{(n-1)} f(0) - s^{(n-2)} f'(0) \dots - f^{(n-1)}(0)$	$f^{(n)}(t)$	n^{th} derivative
$\frac{F(s)}{s}$	$\int_0^t f(u)du$	Integral
$\frac{F(s)}{s^n}$	$\int_0^t \dots \int_0^t f(u)du^n = \int_0^t \frac{(t-u)^{n-1}}{(n-1)!} f(u)du$	n-fold integral
$F(s) \cdot G(s)$	$\int_0^t f(u)g(t-u)du$	Convolution in the time domain


Electronics

Understanding Transfer Functions

$F(s)$	$f(t)$
$\frac{1}{s}$	1
$\frac{1}{s^2}$	t
$\frac{1}{s^n} \quad n = 1, 2, 3, \dots$	$\frac{t^{n-1}}{(n-1)!}, \quad 0!=1$
$\frac{1}{s-a}$	e^{at}
$\frac{1}{s^2 + a^2}$	$\frac{\sin at}{a}$
$\frac{s}{s^2 + a^2}$	$\cos(at)$
$\frac{1}{s^2 - a^2}$	$\frac{\sinh at}{a}$
$\frac{P(s)}{Q(s)}$; $Q(s) = (s - \alpha_1) \dots (s - \alpha_n)$	$\sum_{k=1}^n \frac{P(\alpha_k)}{Q'(\alpha_k)} e^{\alpha_k t}; \quad Q'(\alpha_k) = \frac{dQ(\alpha_k)}{d(s - \alpha_k)}$

Electronics

Understanding Transfer Functions

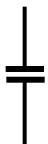


$$Q = C U; \dot{Q} = I = C \dot{U}$$

$$I(s) = s C U(s)$$

$$R_C = \frac{U(s)}{I(s)} = \frac{1}{sC}$$
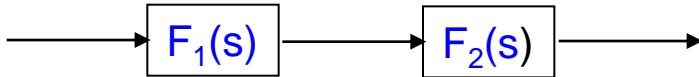
$$T(s) \stackrel{\text{def}}{=} \frac{\text{Output}(s)}{\text{Input}(s)}$$



$$T(s) = F_1(s) \cdot F_2(s) \quad (\text{Convolution})$$




$$U = L \dot{I}$$

$$U(s) = s L I(s)$$


Recall: $s = Q + i\omega$

$$R_L = \frac{U(s)}{I(s)} = sL$$

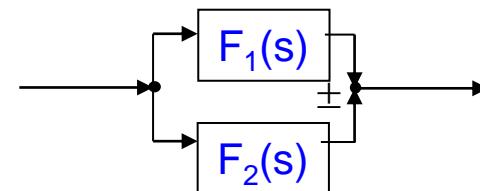

$$T(s) = F_1(s) \pm F_2(s) \quad (\text{Linearity})$$

Feedback (especially: negative feedback)


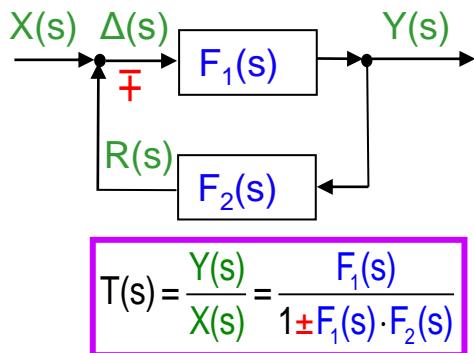


$$\left. \begin{aligned} Y(s) &= F_1(s) \cdot \Delta(s) \\ \Delta(s) &= X(s) - R(s) \\ R(s) &= F_2(s) \cdot Y(s) \end{aligned} \right\} \rightarrow Y(s) = F_1(s) \cdot \{X(s) - (F_2(s) \cdot Y(s))\}$$

Trick: $F_1(s) \rightarrow \infty \Rightarrow T(s) = \pm \frac{1}{F_2(s)} = \pm F_2^{-1}(s)$

Electronics

Understanding Transfer Functions

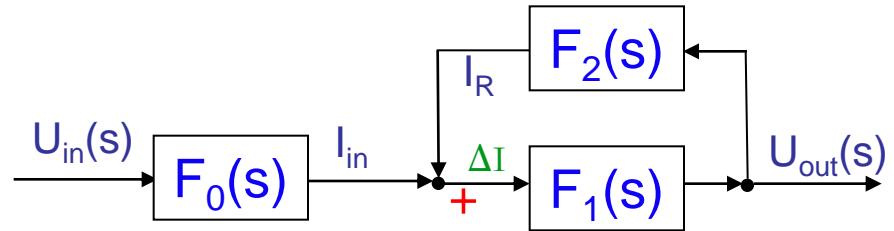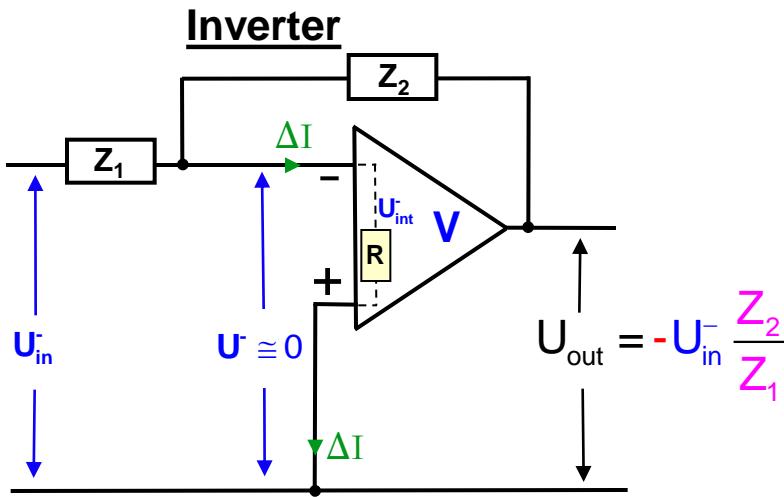

$$T(s) = F_0(s) \cdot \frac{F_1(s)}{1 - F_1(s) \cdot F_2(s)} \xrightarrow{F_1(s) \rightarrow \infty} \frac{F_0(s)}{-F_2(s)} = -\frac{Z_2}{Z_1}$$

with: $F_0(s) = I_{in} / U_{in} = 1/Z_1$


$F_1(s) = -R \cdot V$; R can be considered to convert the

$F_2(s) = I_R / U_{out} = 1/Z_2$ Input Current ΔI to the internal Input Voltage U_{int} .

Electronics


Understanding Transfer Functions

Integrator ($U_{off} = 0$)

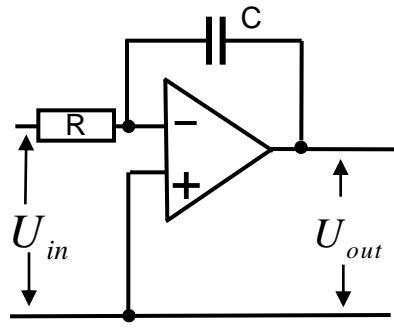


$$U_{out}(s) = -U_{in}(s) \frac{1}{RC} \cdot \frac{1}{s}$$



Differentiator

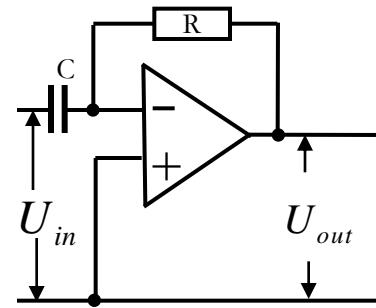
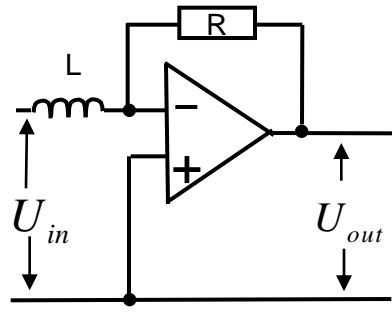
$$U_{out}(s) = -U_{in}(s) \cdot RC \cdot s$$


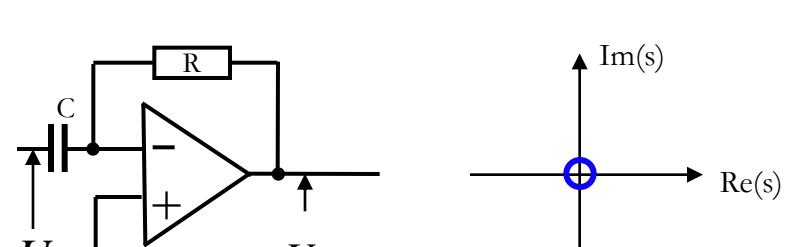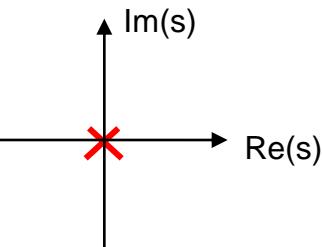
$$U_{out}(s) = -U_{in}(s) \frac{R}{L} \cdot \frac{1}{s}$$



The „s“ in the denominator and nominator determine the dynamics of a system

Electronics

Understanding Transfer Functions

Diagram of a series RLC circuit:

$$U_{in}(t) = U_0 e^{-\frac{t}{T_0}}$$

$$\rightarrow U_{in}(s) = U_0 \frac{1}{s + 1/T_0}$$

$$T(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{R_1}{\frac{1}{sC} + R_1}$$

$$U_{out}(s) = T(s) \cdot U_{in}(s) = U_0 \frac{s}{(s + 1/CR_1)(s + 1/T_0)}$$



$$U_{out}(t) = U_0 \frac{1}{(CR_1 - T_0)} \left(CR_1 e^{-\frac{t}{T_0}} - T_0 e^{-\frac{t}{CR_1}} \right)$$

Graph of the output voltage $U_{out}(t)$ versus time t :

Undershoot


Electronics

The Principle of Pole-Zero Cancellation

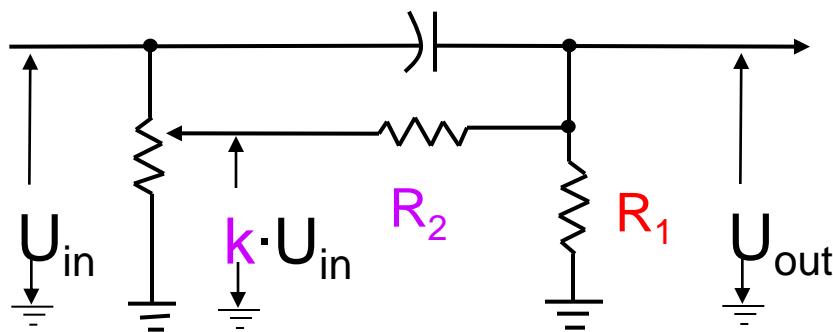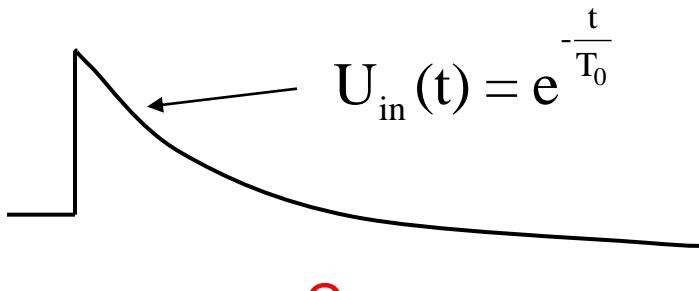

$$R_P = R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$
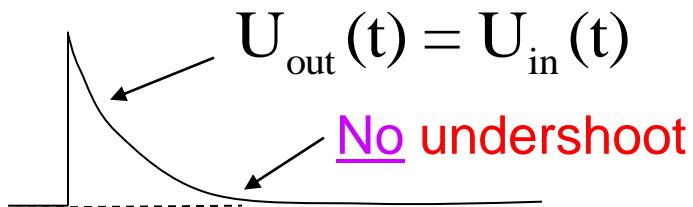
$$T(s) = \frac{s + \frac{k}{R_2 C}}{s + \frac{1}{R_P C}}$$



That is , how it works

Electronics

Understanding Transfer Functions


Stable Systems have Poles only in the negative half plane (imaginary axis included), since **otherwise $p>0$**

Allpasses stand out due to the symmetric position of Poles and Zeros with respect to the imaginary axis.
 $|T(s)| = \text{const.}$; but the phase changes.

Phase minimum systems do not have any Zeros in the right half-plane.


Inferences:

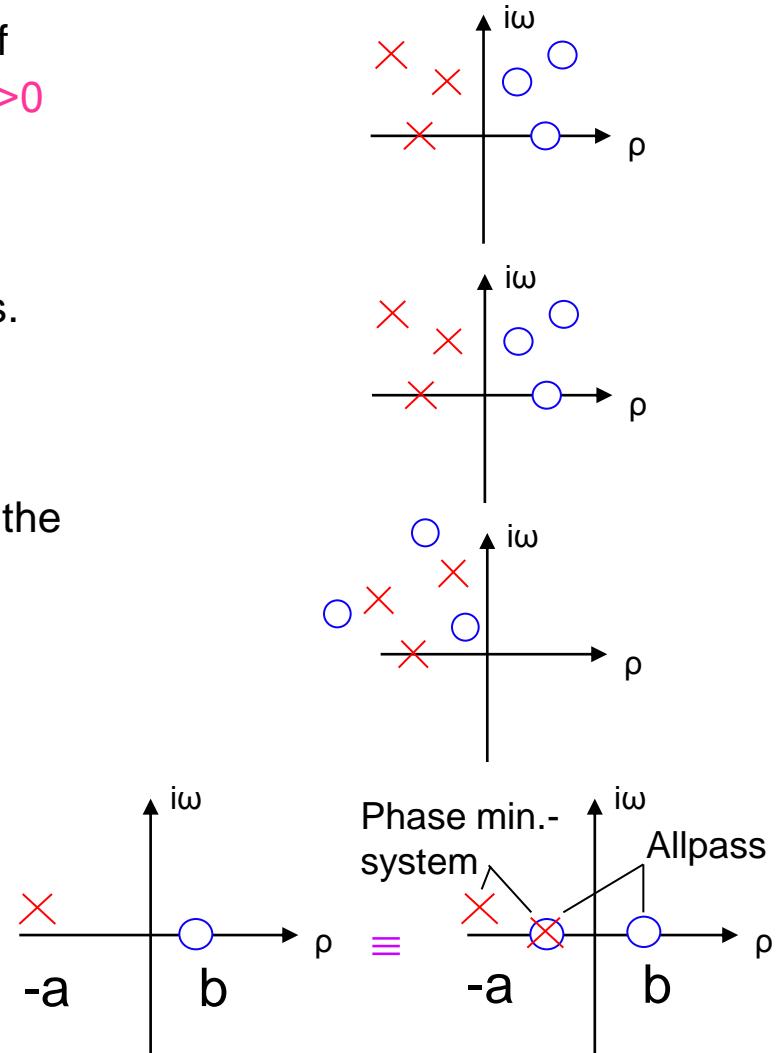All stable linear systems can be set up by allpasses and phase minimum systems.





Electronics

PZ-Scheme of an 3rd Order Allpass

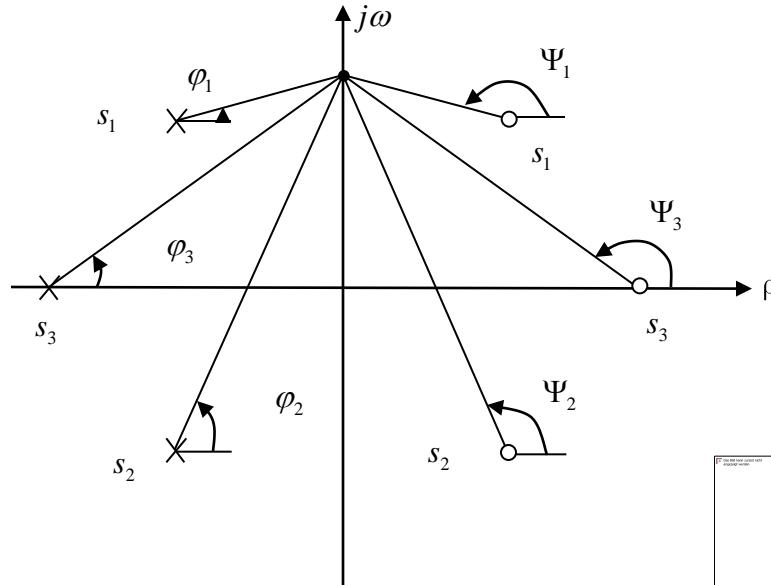


Pole/Zero Applet

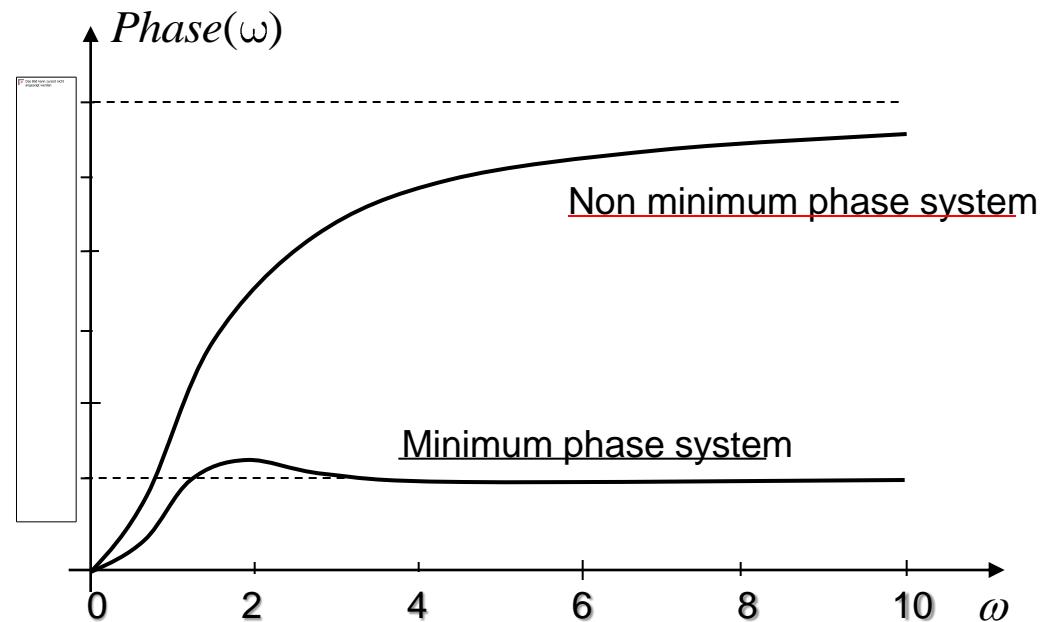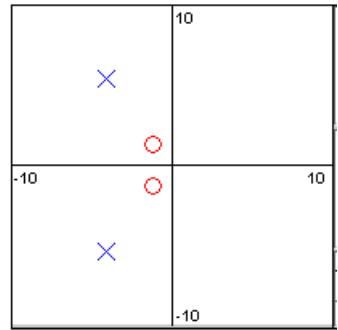

Electronics



Pulse Shaping

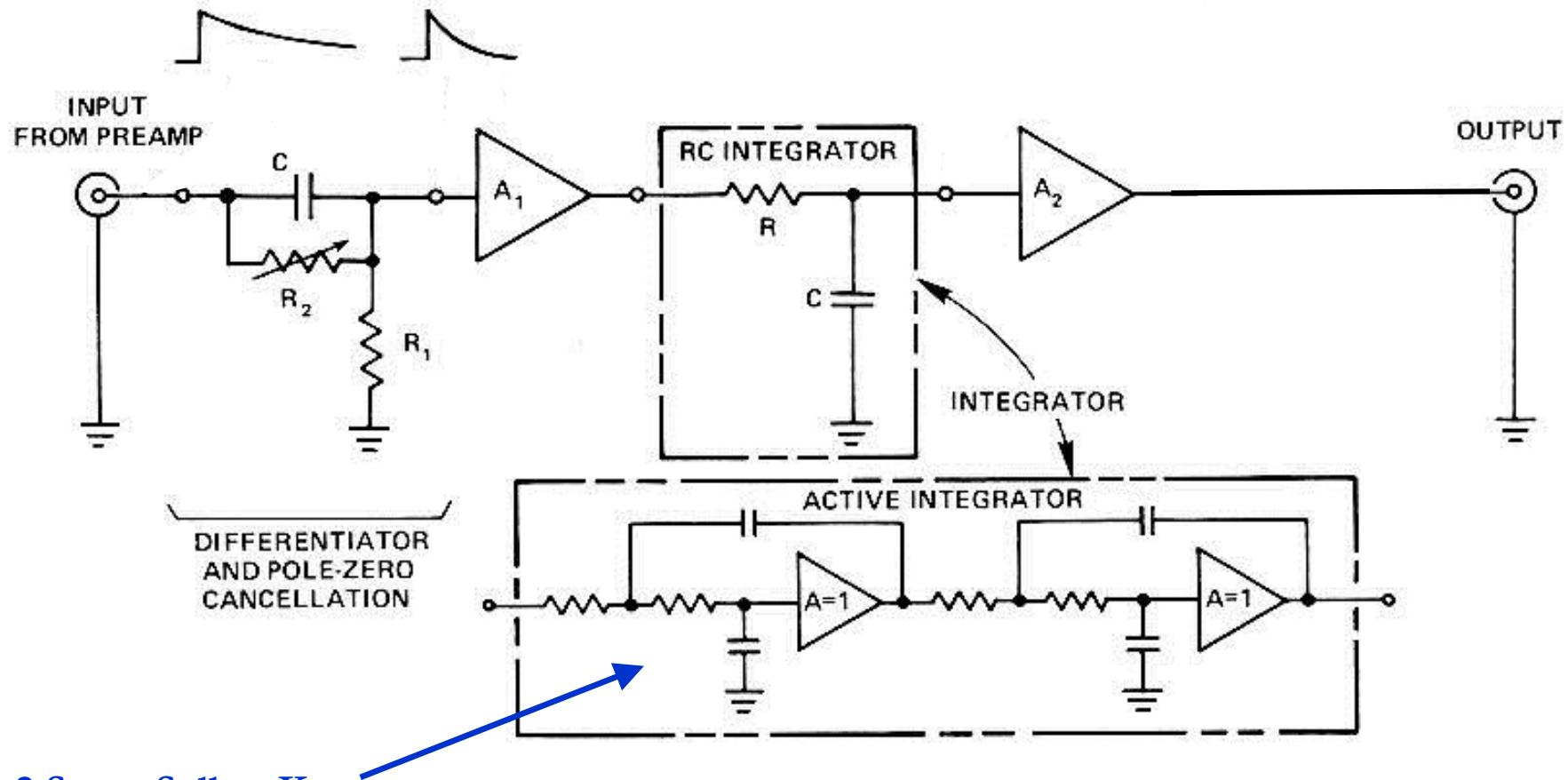

Electronics

The Idea Behind an Optimum S/N-Ratio


Typical (white) Noise Spectrum

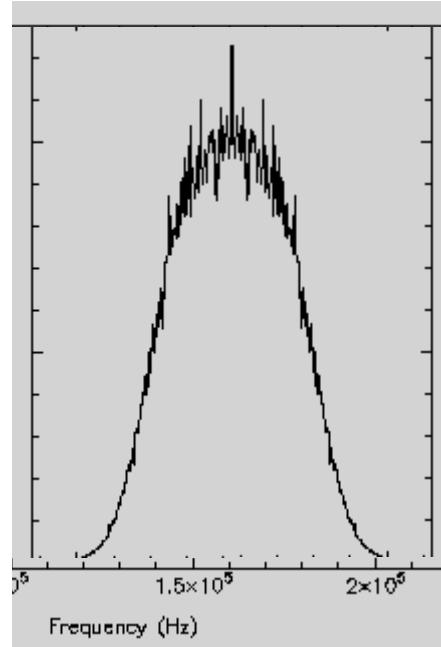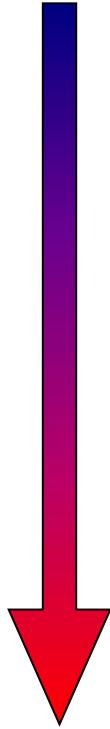

Narrow Bandwidth Noise Spectrum








Electronics

Pulse Shaping

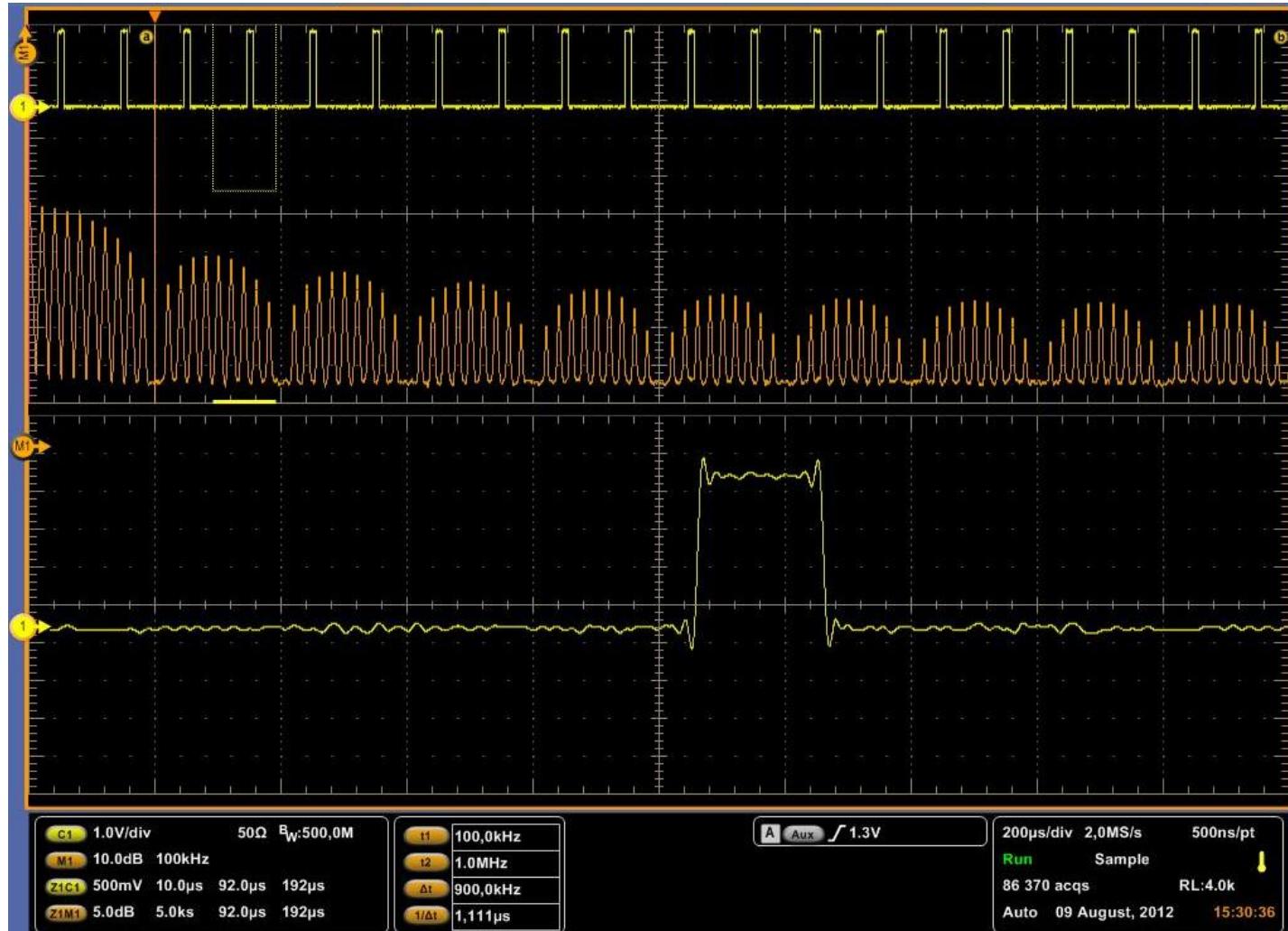







Electronics

Pulse Shaping

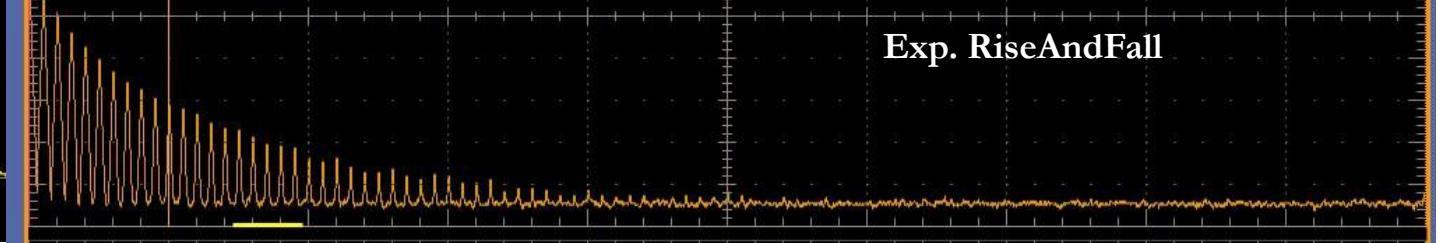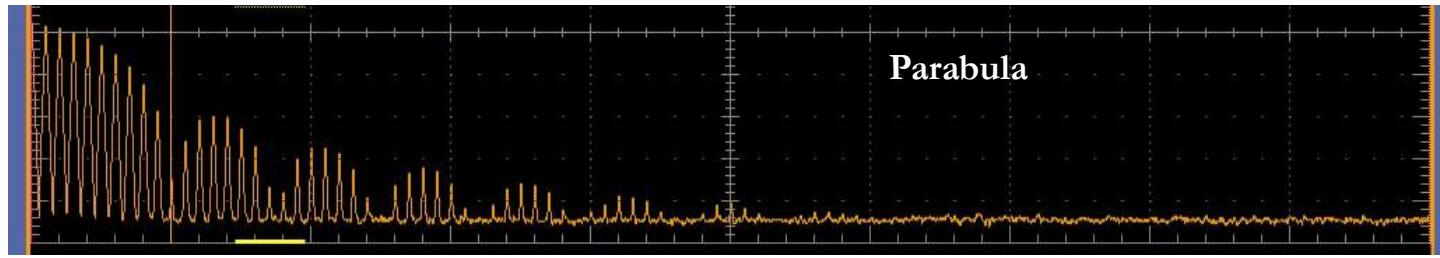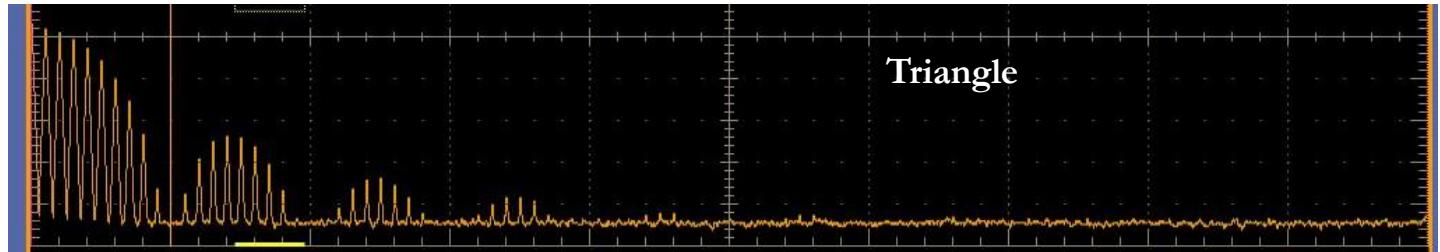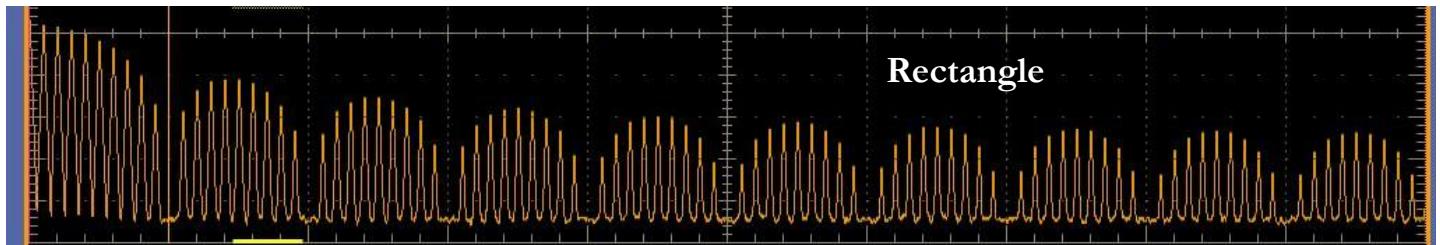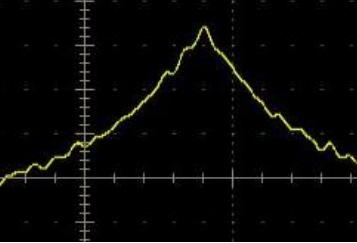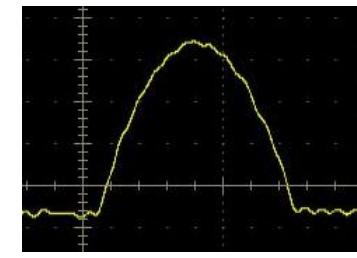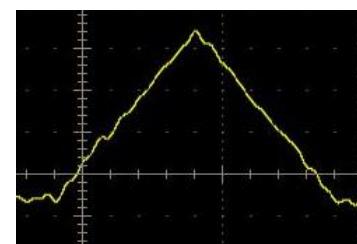

Electronics

Pulse Shaping

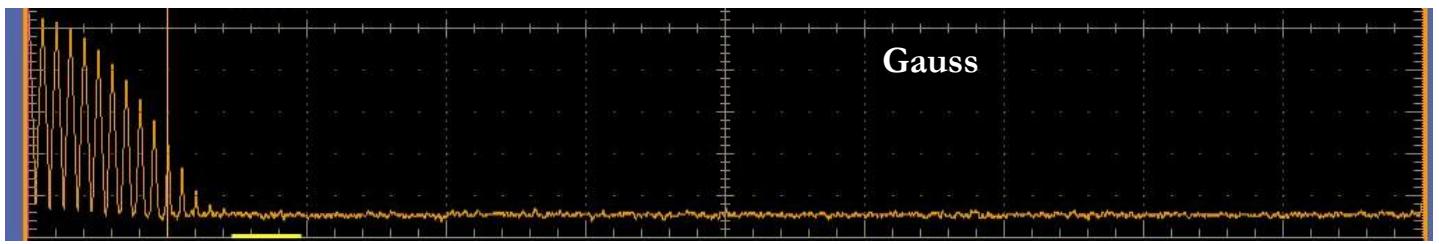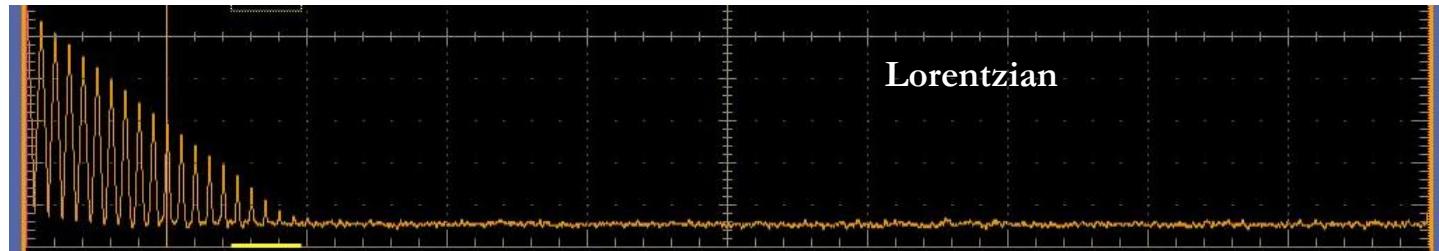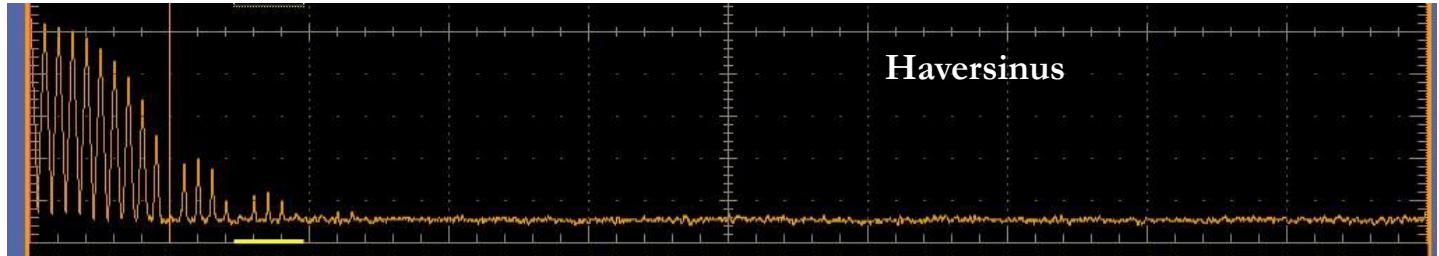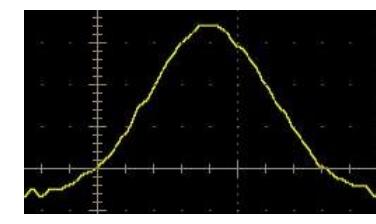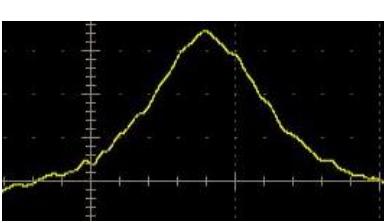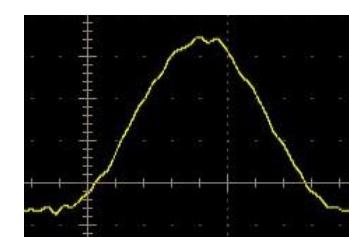

Semi-Gaussian pulse shaping has the fewest harmonics and allows to amplify these pulses with the comparatively smallest bandwidth.
Therefore, all noise outside this bandwidth can be suppressed.




Electronics Summary

Transfer Functions:


- Have a wide field of applications
- Are an universal tool to handle even aperiodic signals
- Give a very basic understanding of systems
- Allow to evaluate or predict the dynamical behavior of a system

You can find further informations (and much more):

www.hiskp.uni-bonn.de

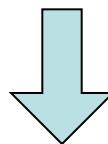

Archive → my lectures

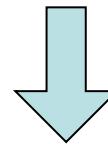


User: student

PW: SSXX


WSXX

Electronics Questions

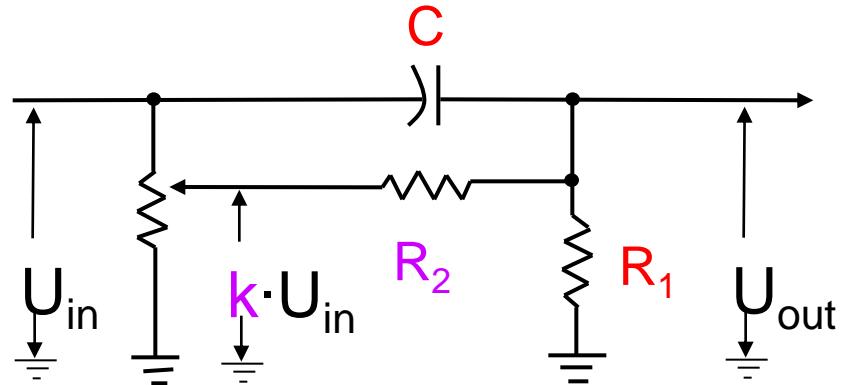- Give two reasons why the P/Z circuit is termed „principal“.



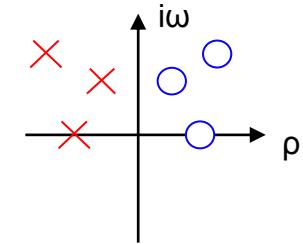- Convince yourself „graphically“ that the amplitude of an Allpass does not depend on frequency.




- Does the „trick“ of linearizing (in negative feedback systems) apply only to operational amplifiers ?

Electronics

The Preamplifier

Q=C U

Q/U Converter

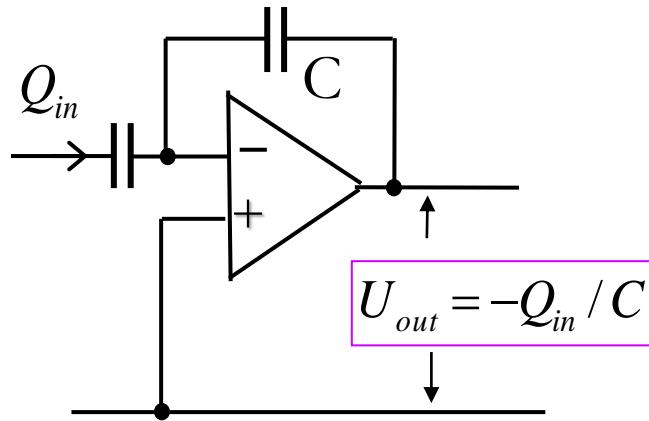

The output voltage is changed, until the charge via **C** compensates Q_{in} from the input

Electronics

Appendix A1 (Backtransform)

$$U_{out}(s) = T(s) \cdot U_{in}(s) = U_0 \frac{s}{(s + 1/CR_1)(s + 1/T_0)}$$


$$U_{out}(t) = U_0 \cdot \left\{ \frac{-1/CR_1}{-1/CR_1 + 1/T_0} e^{-1/CR_1} + \frac{-1/T_0}{-1/T_0 + 1/CR_1} e^{-1/T_0} \right\}$$

$$U_{out}(t) = U_0 \cdot \left\{ \frac{-T_0}{-T_0 + CR_1} e^{-1/CR_1} + \frac{-CR_1}{-CR_1 + T_0} e^{-1/T_0} \right\}$$

$$U_{out}(t) = U_0 \cdot \frac{1}{CR_1 - T_0} \{ CR_1 e^{-1/T_0} + T_0 e^{-1/CR_1} \} \quad \text{q.e.d.}$$

Electronics

Appendix A2 (P/Z Calculation)

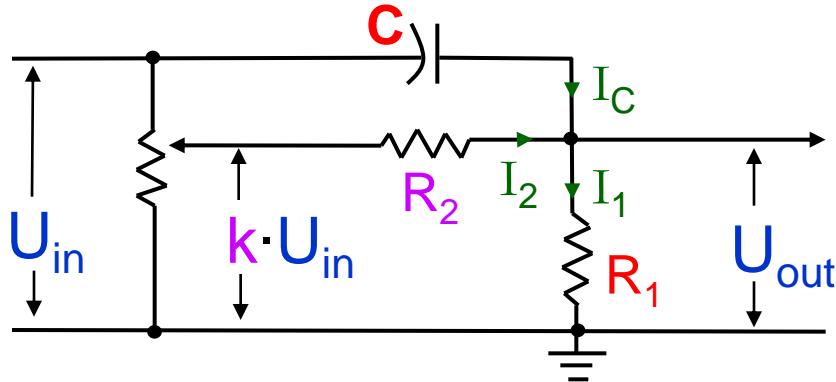

Start with: $I_1 = I_C + I_2$

Recall: $U_{out} = R_1 \cdot I_1 = R_1(I_C + I_2)$

$$U_{out}(s) = R_1 \left\{ \frac{1}{R_2} [k \cdot U_{in}(s) - U_{out}(s)] + C[sU_{in}(s) - sU_{out}(s)] \right\}$$

$$U_{out}(s) \left[1 + \frac{R_1}{R_2} + sCR_1 \right] = U_{in}(s) \left[k \frac{R_1}{R_2} + sCR_1 \right]$$

$$T(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{\frac{kR_1}{R_2} + sCR_1}{1 + \frac{R_1}{R_2} + sCR_1} = \frac{-\frac{k}{R_2C} + s}{(\frac{1}{R} + \frac{1}{R})\frac{1}{C} + s} = \frac{s + \frac{k}{R_2C}}{s + \frac{1}{R_nC}}$$

q.e.d.

Electronics

Appendix A3 (P/Z Circuit Considerations – Reality)

$$T(s) = \frac{s + \frac{k}{R_2 C}}{s + \frac{1}{R_p C}}$$


In order to have: $\frac{k}{R_2} = \frac{1}{R_p}$

recall that $R_p \leq R_2$

Therefore: $\frac{k}{R_2} \geq \frac{1}{R_2}$ or: $k \geq 1$

But since **k** is always a fraction of 1 this constitutes a **contradiction**.

Solution:

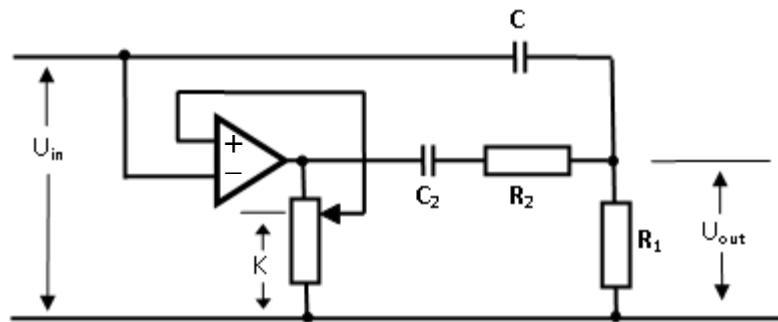


But what is with **C₂** ?


One can always find for any given ω a C , so that $R_C = \frac{1}{sC} \xrightarrow{\rho=0} \frac{1}{i\omega C} \ll R_2$

Electronics

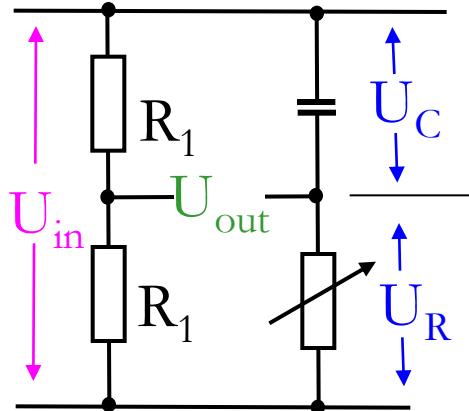Appendix B (Scheme of an 1st Order Allpass)



Thales' Circle

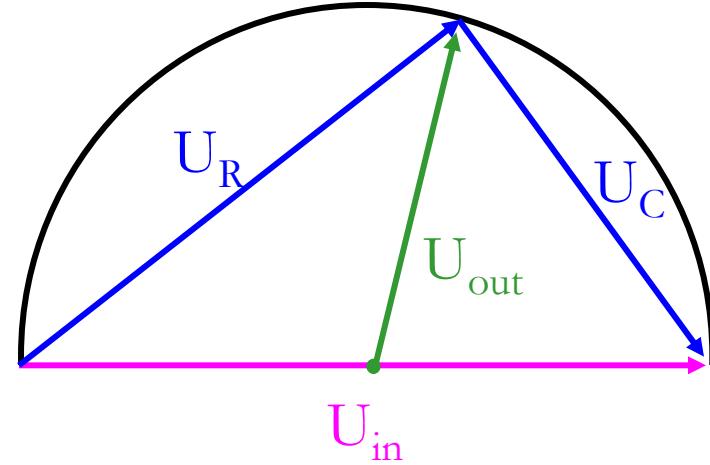

$$U_{\text{out}} = U_{R_1} - U_C = \frac{1}{2} U_{\text{in}} - \frac{R_C}{R + R_C} U_{\text{in}}$$

$$T_C(s) = \frac{U_{\text{out}}}{U_{\text{in}}} = \frac{1}{2} \frac{R + R_C - 2R_C}{R + R_C} = \frac{1}{2} \cdot \frac{R - 1/sC}{R + 1/sC} = \frac{1}{2} \cdot \frac{sRC - 1}{sRC + 1}$$

Electronics

Appendix C (Sallen-Key Amplifier)

$$U_{\Sigma} \cdot \frac{sC}{sRC + 1} = I_{\Sigma} = \frac{U_{in} - U_{\Sigma}}{R} + (U_{out} - U_{\Sigma}) \cdot sC$$

$$= \frac{U_{in} - U^+(1 + sRC)}{R} + (U_{out} - U^+(1 + sRC)) \cdot sC$$

$$U^+ \left[(1 + sRC) \cdot \frac{sC}{sRC + 1} + \frac{1 + sRC}{R} + (1 + sRC) \cdot sC \right] = \frac{U_{in}}{R} + U_{out} \cdot sC$$


$$U_{out} = V \cdot \frac{\frac{U_{in}}{R} + U_{out} \cdot sC}{sC + \frac{1 + sRC}{R} + (1 + sRC) \cdot sC} \stackrel{\text{def}}{=} \frac{U_{in}/R + U_{out} \cdot sC}{\text{Nenner}}$$

$$U_{out} \left(1 - \frac{VsC}{\text{Nenner}} \right) = \frac{V}{R} \cdot \frac{U_{in}}{\text{Nenner}}$$

$$T(s) = \frac{V}{R} \cdot \frac{1}{\text{Nenner}} \cdot \left(\frac{\text{Nenner} - VsC}{\text{Nenner}} \right)$$

$$T(s) = \frac{V}{R} \cdot \frac{1}{\text{Nenner} - VsC} = \frac{V}{sRC + 1 + sRC + (1 + sRC) \cdot sRC - VsRC}$$
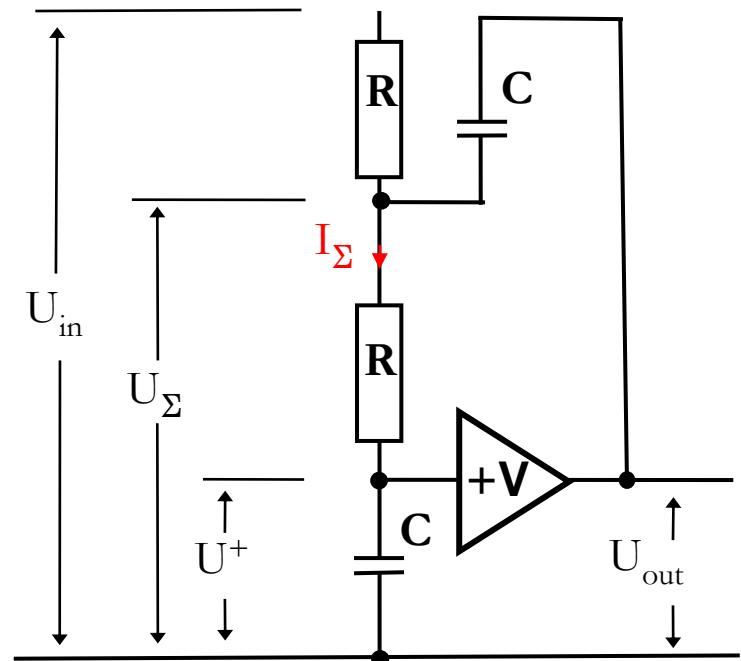
$$= \frac{V}{1 + 3sRC - VsRC + (sRC)^2} = \frac{V}{1 + sRC \cdot (3 - V) + (sRC)^2}$$



Electronics

Appendix D (Nonlinear Systems)

Given:

Set of m non-linear differential equations:

$$\vec{y} = f(\vec{x}, \vec{u}) \quad \text{with: } \vec{x} - n \text{ Variables}$$

$$\vec{u} - \ell \text{ Parameters}$$

Expand f for the (operating) point A:

$$\vec{y} \approx f(\vec{x}_A, \vec{u}_A) + \frac{\partial f}{\partial \vec{x}}_{|A} \cdot \delta \vec{x} + \frac{\partial f}{\partial \vec{u}}_{|A} \cdot \delta \vec{u} + \text{Higher order terms; } m \leq n$$


$m \times n$ matrix \mathbf{F} $m \times \ell$ matrix \mathbf{G}

$$= \mathbf{f}(\vec{x}_A, \vec{u}_A) + \mathbf{F} \cdot \delta \vec{x} + \mathbf{G} \cdot \delta \vec{u}$$


This is a system of coupled linear differential equations, which can be algebraized by means of the Laplace transform.

Electronics

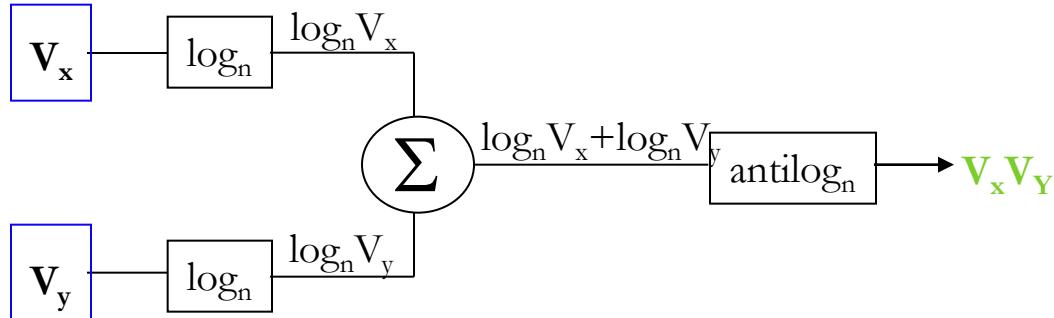Example Ia (Principle of a Log-Antilog Multiplier)



Log - Amp

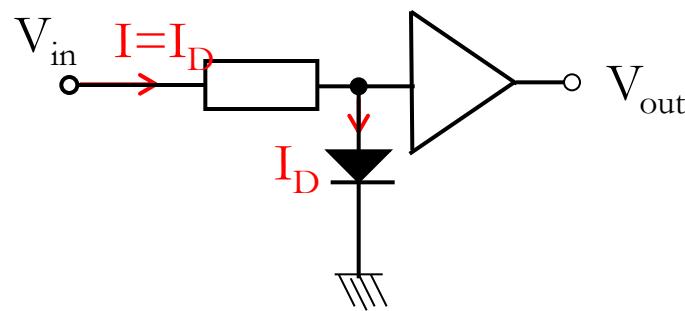


$$I_D \propto e^{-\frac{U}{U_T}} \Rightarrow U \propto U_T \ln I_D$$

Electronics

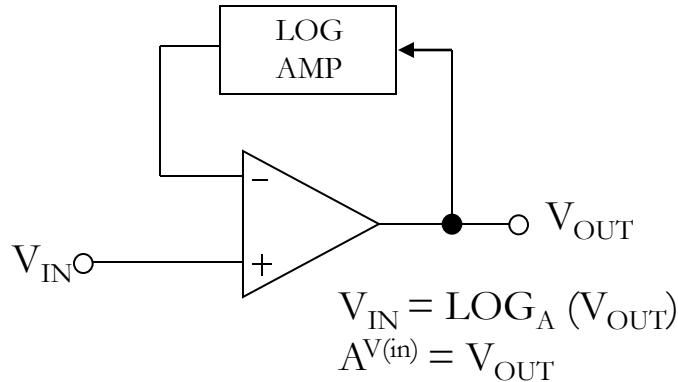Example Ib (Principle of a Log-Antilog Multiplier)

Log Amp as a negative feedback element
results in a Anti-Log-Amplifier:




$$\begin{aligned} T(s) &= \frac{F(s)}{1 + F(s)G(s)} \\ &= \frac{1}{1/F(s) + G(s)} \xrightarrow{F(s) \rightarrow \infty} \mathbf{1/G(s) = G^{-1}(s)} \end{aligned}$$

Example of an analog multiplier: Amplitude modulation


Carrier frequency: V_x



Modulated signal: V_y


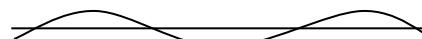


Output (Modulated carrier): $V_x V_y$

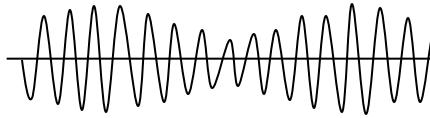

Electronics


Example IIa (Principle of a Sonar)

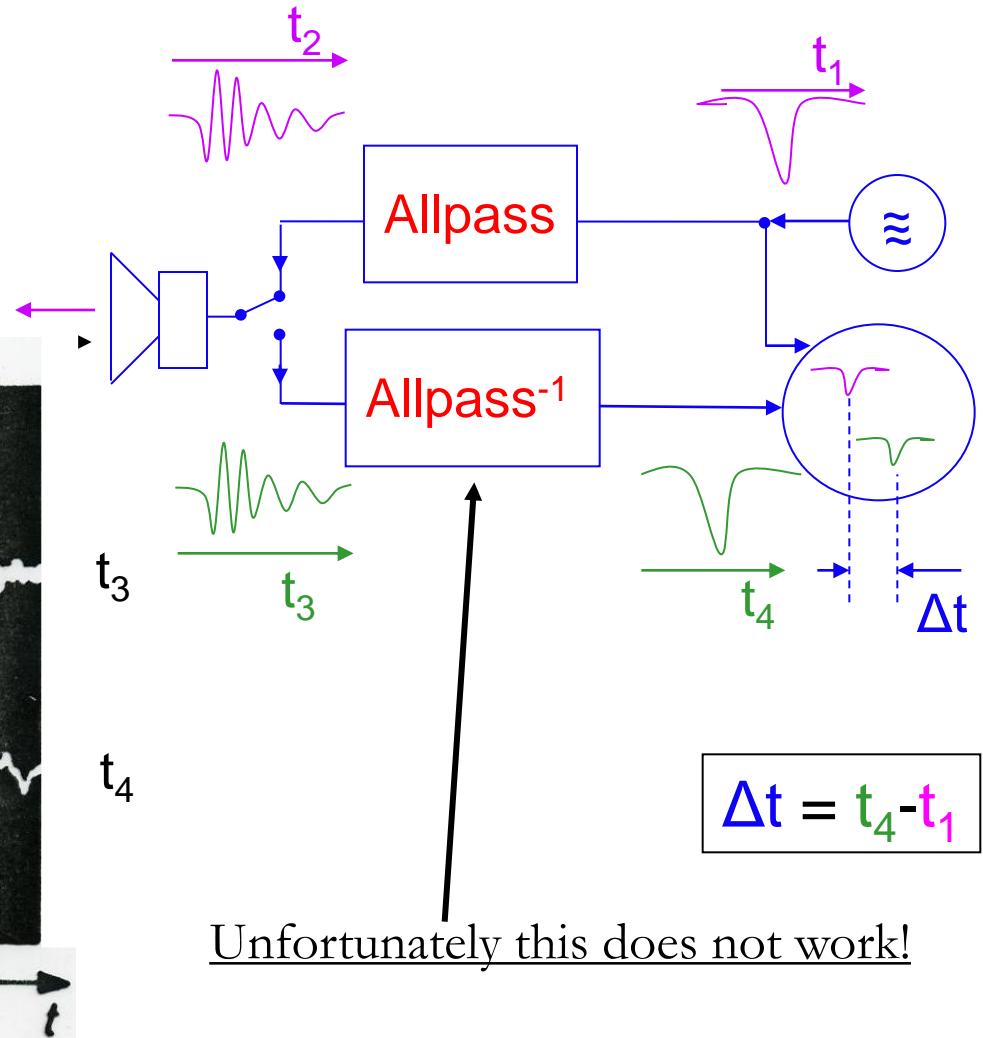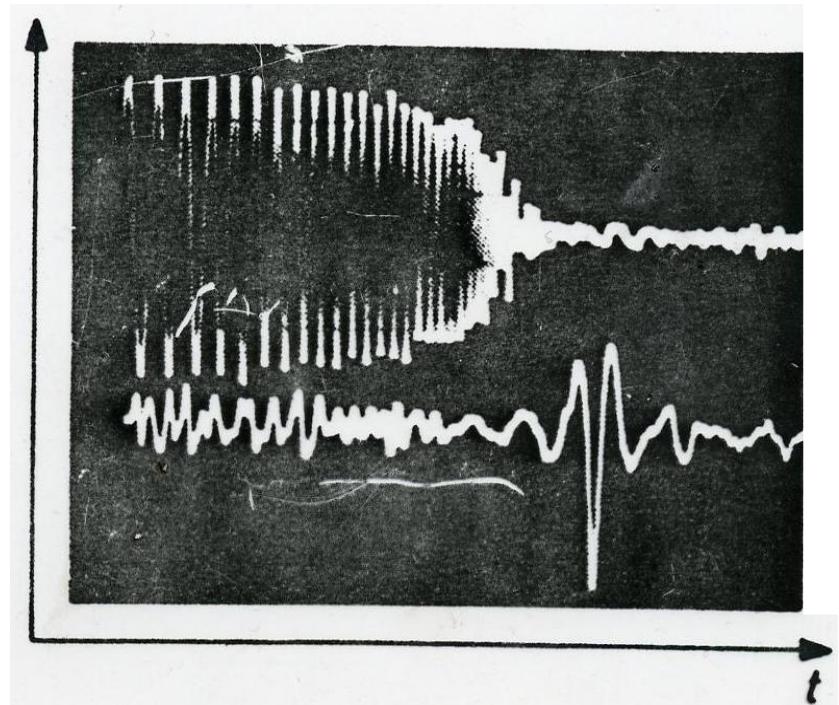

Unfortunately this does not work!

Electronics


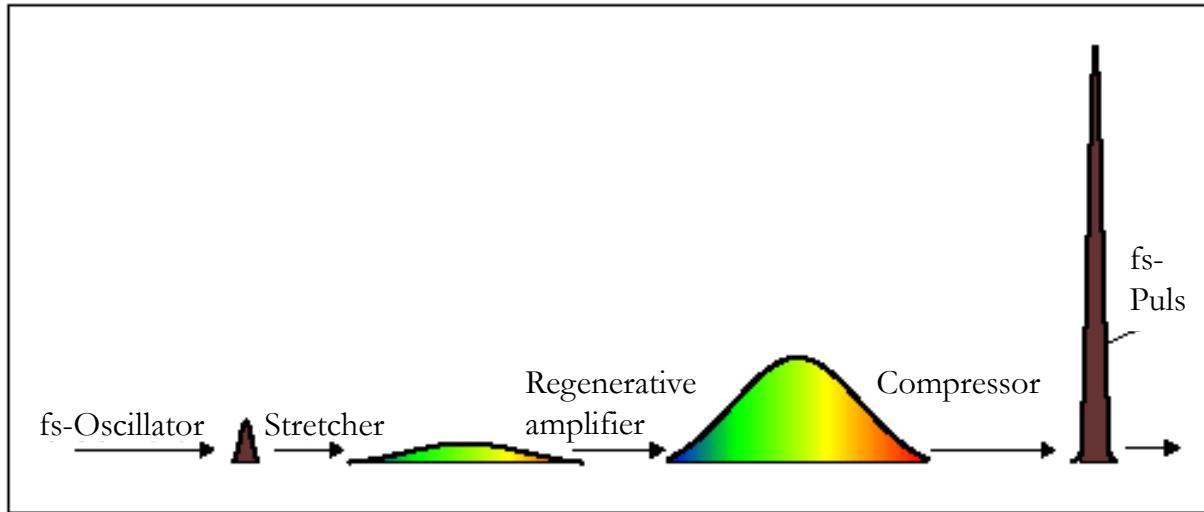
Example IIb (Chirped Pulse Amplification (CPA))



Principle of the CPA : High peak intensities within the amplifier optics are avoided by timewise and spatial dilatation of the pulses.

Electronics

Example III (Linearizing Systems)

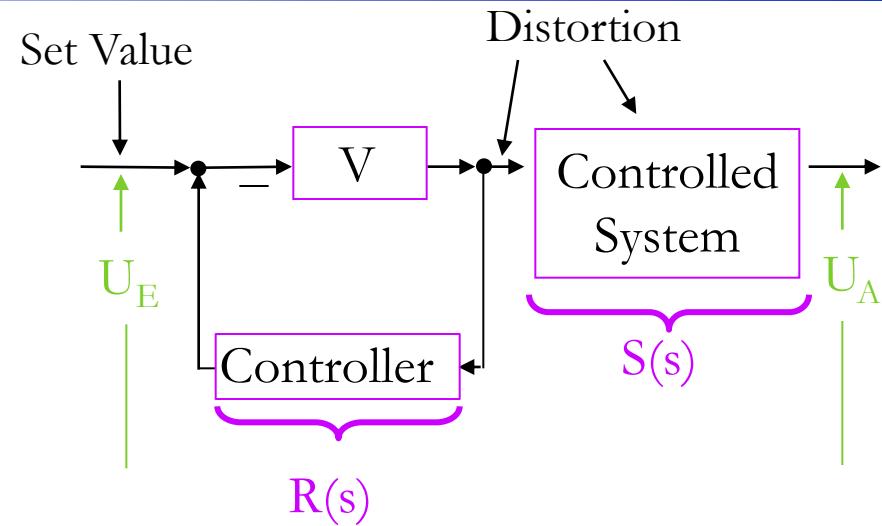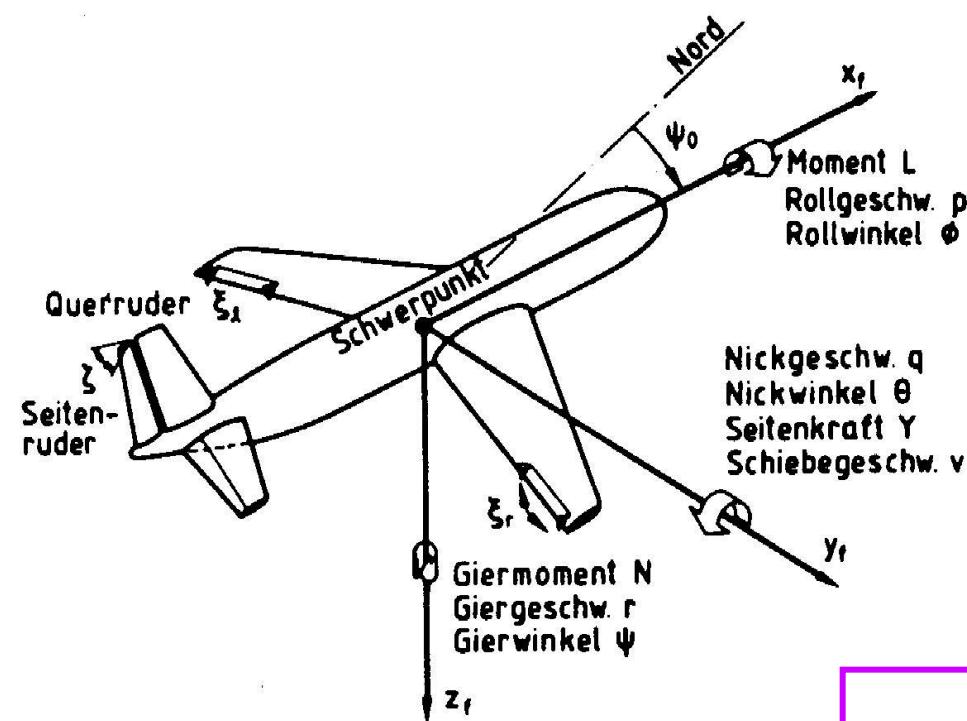

$$T(s) = \frac{V}{I + V \cdot R} S = \frac{V \cdot S}{I + V \cdot R} \xrightarrow{v \rightarrow \infty} \frac{S}{R}$$

→ the dynamics of $T(s)$ can be determined by the position of the Pole/Zero-distribution of $R(s)$.